


# INDUCTIVE AND CAPACITIVE COUPLING

MATTHEW BECK

## NOMENCLATURE

$\omega_r$	Resonant cavity frequency
$C_{\text{Res}}$	Resonator Capacitance
$C_c$	Coupling Capacitance
$L_{\text{Res}}$	Resonator Inductance
$M$	Coupling Inductance
$Q_c^C$	Capacitive coupling quality factor
$Q_c^L$	Inductive Coupling quality factor

## INDUCTIVE COUPLING

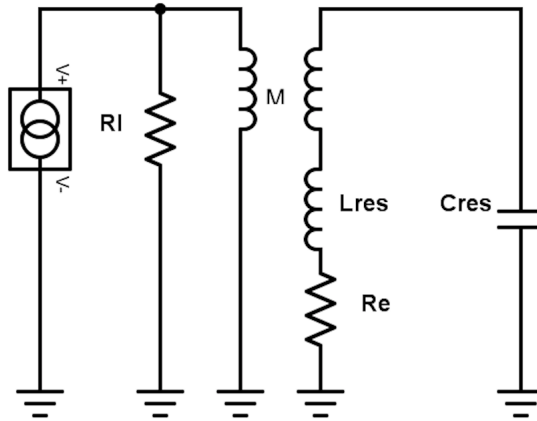

We begin by defining the noise current power spectral density for the input side of the circuit.

$$S_I = \frac{4k_bT}{R_l} \quad (1)$$

The induced noise voltage on the resonator is then

$$S_V = 4k_bTR_e \quad (2)$$

We can relate (1) and (2) via the mutual inductance,  $M$  and the frequency.

$$\frac{4k_bT}{R_l}(\omega M)^2 = 4k_bT R_e \quad (3)$$

Solving for  $R_e$  yields


$$R_e = \frac{(\omega M)^2}{R_l} \quad (4)$$

The inductive coupling quality factor is then defined as

$$Q_c^L = \frac{\omega L_{\text{res}}}{R_e} = \frac{L_{\text{res}} R_l}{\omega M^2} = \frac{2Z_0 L_{\text{res}}}{\omega M^2} \quad (5)$$

Where the substitution  $R_l = 2Z_0$  has been made.

#### CAPACITIVE COUPLING

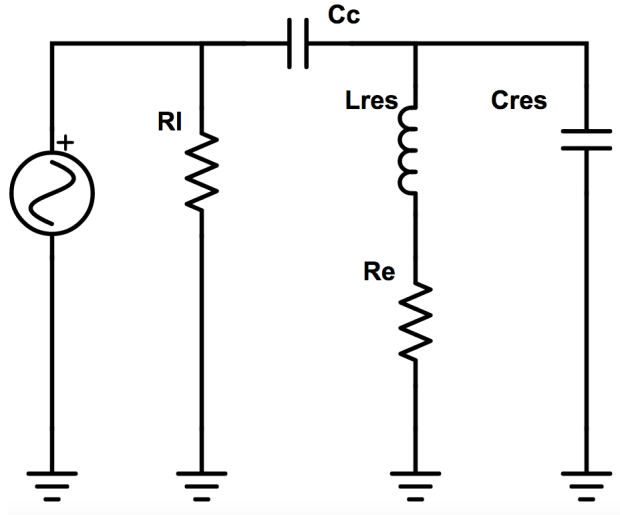

We begin by defining the noise voltage power spectral density for the input side of the circuit

$$S_V = 4k_bT R_l \quad (6)$$

This induces a noise current in the resonator of the form

$$S_I = \frac{4k_bT}{R_e} \quad (7)$$

This can be equated via the coupling impedance

$$\frac{S_I}{(\omega C_c)^2} = S_V \quad (8)$$

$$\frac{4k_b T}{R_e(\omega C_c)^2} = 4k_b T R_l \quad (9)$$

$$R_e = \frac{1}{(\omega C_c)^2 R_l} \quad (10)$$

We can then define the coupling quality factor as

$$Q_c^C = \omega R_e C \quad (11)$$

$$= \frac{\omega C}{(\omega C_c)^2 R_l} \quad (12)$$

$$= \frac{C}{2Z_0 \omega C_c^2} \quad (13)$$

Where we have again made the substitution  $R_l = 2Z_0$ . One can see that (13) matches with the result obtained in Goppl, et al. in the limit that  $(\omega C_c R_l)^2 \ll 1$